



STANFORD UNIVERSITY

Stanford Center for Professional Development

# HOMEWORK ROUTE FORM

Stanford Center for Professional Development Student Information

Course No. EE214B Faculty / Instructor Name Boris Murmann Date 12 Feb 2016

Student Name Samuel Lenius Phone 7013880568

Company Google Inc Email

City Mountain View State CA Country USA

Check One:  Homework #: 5  Midterm  Other

The email address provided on this form will be used to return homework, exams, and other documents and correspondence that require routing.

Total number of pages faxed including cover sheet 12

Date Received by the Stanford Center for Professional Development	<b>For Stanford Use Only</b>  Date Instructor returned graded project  Score/Grade: (to be completed by instructor or by teaching assistant)	Date the Stanford Center for Professional Development returned graded project:  <b>STANFORD USE ONLY</b>
---	---	--

Please attach this route form to ALL MATERIALS and submit ALL to:

**Stanford Center for Professional Development**

496 Lomita Mall, Durand Building, Rm 410, Stanford, CA 94305-4036

Office 650.725.3015 | Fax 650.736.1266 or 650.725.4138

For homework confirmation, email [scpd-distribution@lists.stanford.edu](mailto:scpd-distribution@lists.stanford.edu)

<http://scpd.stanford.edu>

1) 9.2) Signal 150 mV<sub>rms</sub>, in series with noise voltage

a) SNR for 1mV<sub>rms</sub>,

$$\text{SNR} = \frac{\bar{V}_S}{V_n^2} = \frac{150^2}{1^2} = 22500 = [43.5 \text{ dB}]$$


b) 70dB, how small must noise be?

$$70 \text{ dB} = 20 \log_{10} \left( \frac{V_{\text{sig}}}{V_{\text{noise}}} \right)$$

$$10^{\frac{70}{20}} = \frac{V_{\text{sig}}}{V_{\text{noise}}} \quad V_{\text{noise}} = \frac{V_{\text{sig}}}{10^{\frac{70}{20}}} =$$

$$[47.4 \mu\text{V}_{\text{rms}}]$$

2) 9.19 )

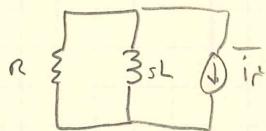

$$R \parallel L \Rightarrow Z_C = \frac{R \cdot sL}{R + sL}$$

$i_{\text{in}}(t)$  = current in inductor

Current divider

$$i_L = \frac{R}{sL + R} \cdot i_{\text{in}}(t)$$

$$\bar{I}_n = \frac{4kT}{R}$$

$$i_L = \frac{1}{1 + sL/R} \cdot i_{\text{in}}(t) \Rightarrow f_o = \frac{1}{2\pi L/R}$$

$$f_o = \frac{R}{2\pi L}$$

ENBW

$$f_n = \frac{\pi}{2} f_o = \frac{R}{4L}$$

$$\bar{I}_R = \frac{4kT}{R} \cdot \frac{R}{4L} = \frac{kT}{2}$$

3)  $\gamma = 0.85 \quad T = 300K$

$$I_d = 571 \mu A \quad g_m = 4.017 mS \quad g_o = 123 \mu S \Rightarrow r_o = 8.13 k\Omega$$

a) Calculate thermal noise

$$R_L = 1k\Omega \quad R_S = 10k\Omega \quad R_L || r_o = 890\Omega$$

$$A_{v_o} = g_m \cdot (R_L || r_o) = 3.57$$

$$\overline{V_{T_{R_L}}^2} = 4kT R_L = 16.56 nV^2/Hz \rightarrow \text{output}$$

$$\overline{V_{T_{R_S}}^2} = 4kT R_S = 165.6 nV^2/Hz \rightarrow \text{input}$$

$$\overline{I_d^2} = 4kT \gamma g_m = 56.54 pA^2/Hz \rightarrow \text{output}$$

$$\overline{V_{d_o}^2} = \overline{I_d^2} \cdot (R_L || r_o)^2 = 44.8 nV^2/Hz \rightarrow \text{output}$$

Input referred

$$\overline{V_{T_{R_L}}^2} = \overline{V_{T_{R_S}}^2} / A_{v_o}^2 = 1.3 nV^2/Hz$$

$$\overline{V_{D_i}^2} = 3.51 nV^2/Hz$$

Total input referred noise

$$\overline{V_{N_i}^2} = \overline{V_{T_{R_S}}^2} + \overline{V_{T_{R_L}}^2} + \overline{V_{d_i}^2} = 170.4 nV^2/Hz \text{ half scaling fit}$$

differential circuit  $\overline{V_{N_i}^2} = 340.8 nV^2/Hz = 18.46 nV/\sqrt{Hz}$

b) Midband noise =  $339.2 nV^2/Hz \rightarrow$  extremely good estimate  
 $0.47\% \text{ error at } 10\text{MHz}$

Low freq error due to flicker noise on gates

High freq error due to capacitances in mosfets and load

3)

c) 100 Hz - 100 MHz at output

$$340.8 \text{ nV}^2/\text{Hz} \cdot A_{v_o}^2 = 4.343 \text{ nV}^2/\text{Hz} = \overline{V_{T_o}^2}$$

$$\sqrt{\overline{V_{T_o}^2}} \cdot \Delta f = 4340 \mu\text{V}^2 = 659 \mu\text{V}_{\text{rms}}$$


d) Calculated noise 650.9  $\mu\text{V}_{\text{rms}}$  error: 1.24%


Plot attached

flicker noise is completely insignificant

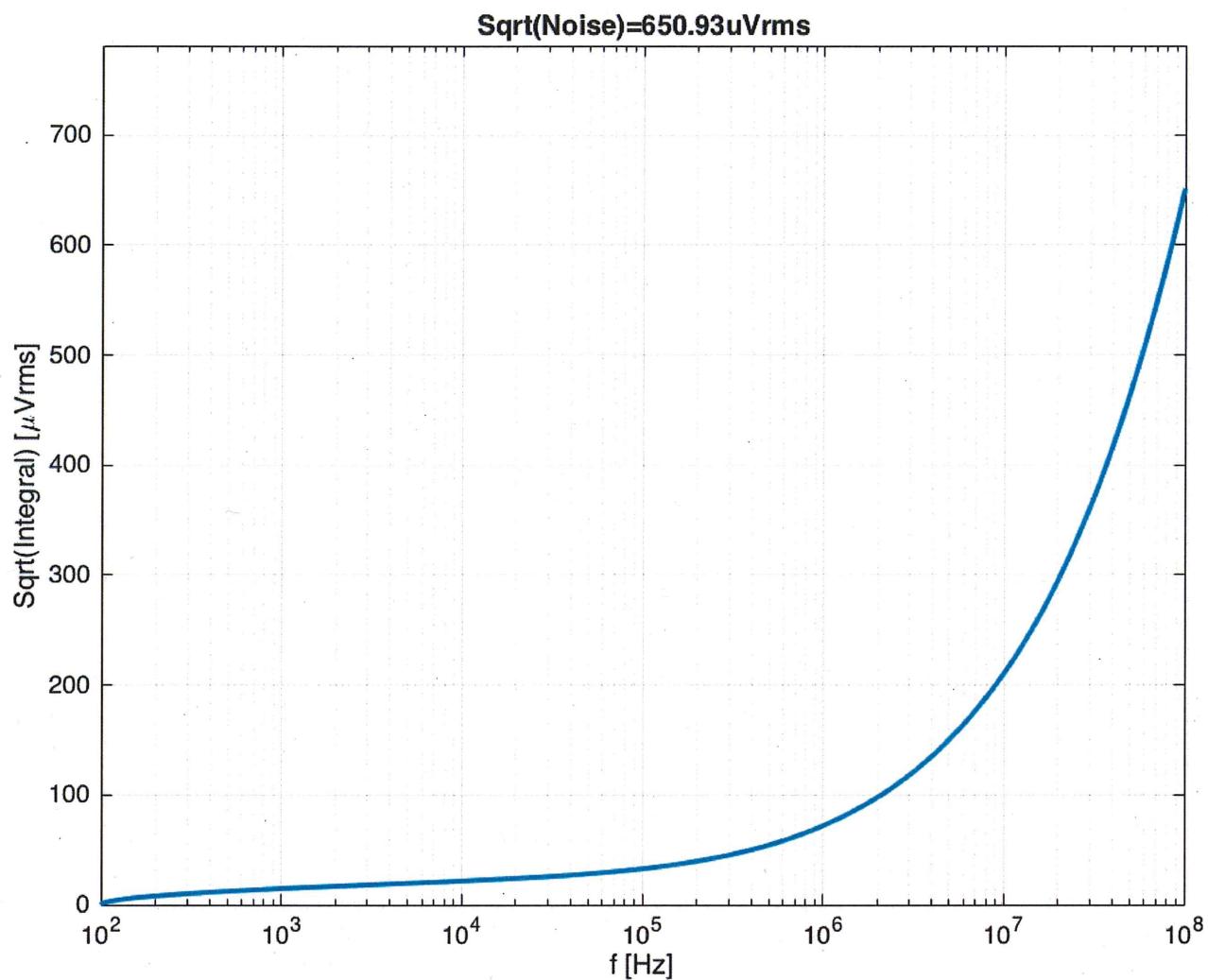
e) Signal power =  $\sqrt{2} \overline{V_A} = 14.14 \text{ mV}_{\text{rms}}$ 

$$\text{SNR} = 20 \log_{10} \left( \frac{\text{Rms Signal}}{\text{Rms noise}} \right) \approx 26.7 \text{ dB}$$



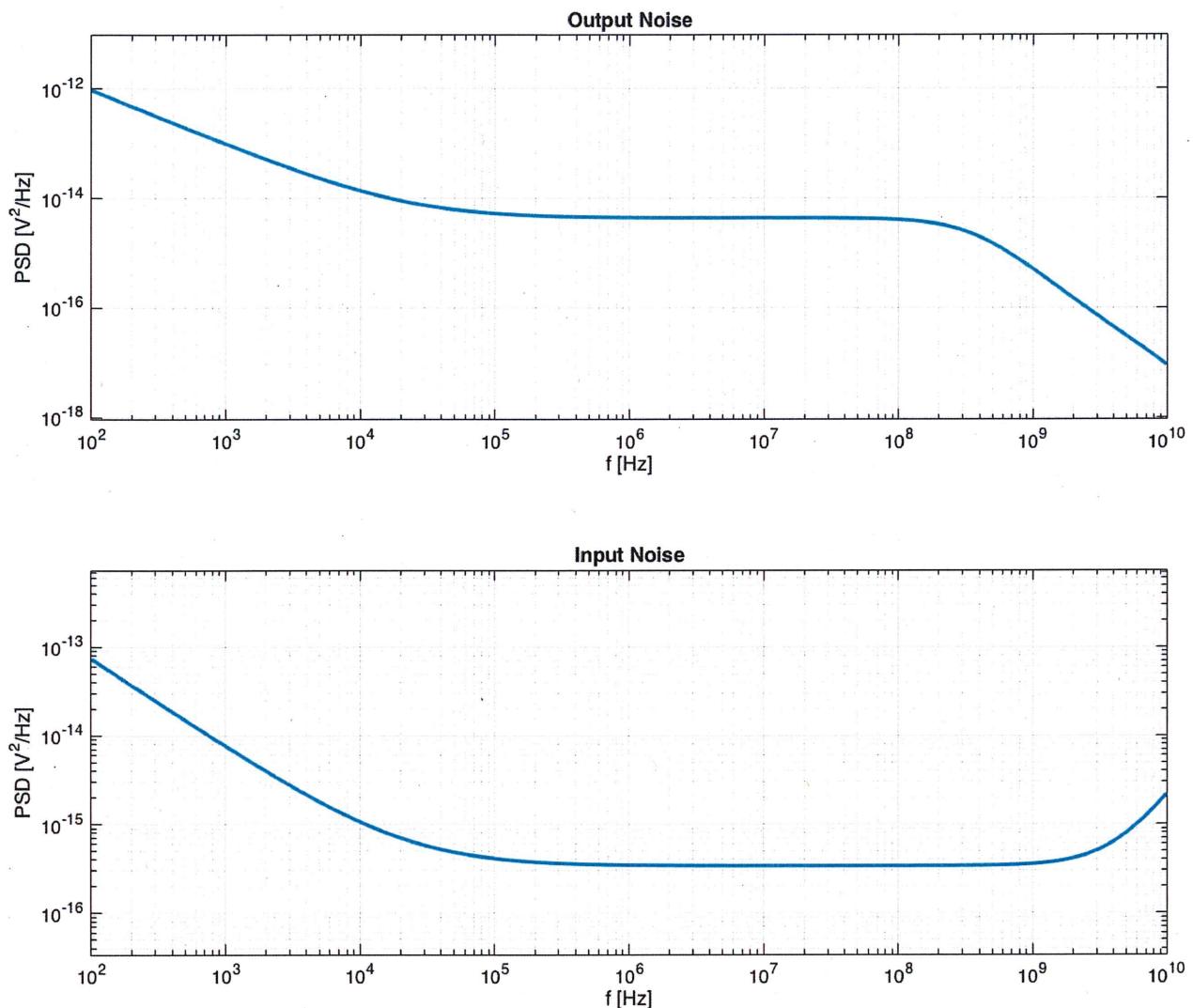

4) a)

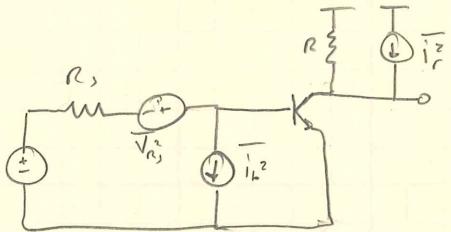

$$\frac{\overline{V_o^2}}{\Delta f} = 4kT \left( R_s + \frac{gmR_s^2}{2\beta} + \frac{R}{gm^2R_L} + \frac{1}{2gm} \right)$$

Collector current that minimizes noise

$$gm = \frac{I_c}{V_T} \quad V_T = \frac{kT}{q} \Rightarrow gm = \frac{I_c \beta}{kT}$$

$$4kTR_s + \frac{4kT I_c R_s^2}{V_T \cdot 2\beta} + \frac{4kTR}{(\frac{I_c \beta}{V_T})^2} + \frac{4kT}{2 \frac{I_c}{V_T}}$$

$$4kTR_s + \frac{Z_B I_c R_s^2}{\beta} + \frac{4kTR}{\frac{I_c^2 \beta^2}{k^2 T^2}} + \frac{2kT}{\frac{I_c \beta}{kT}}$$

$$4kTR_s + I_c \left( \frac{Z_B R_s^2}{\beta} \right) + \frac{1}{I_c^2} \left( \frac{4k^3 T^3 R}{q^2} \right) + \frac{1}{I_c} \left( \frac{2k^2 T^2}{q} \right)$$

$$a = 4kTR_s, \quad b = \frac{Z_B R_s^2}{\beta}, \quad c = 4V_T^2 kTR, \quad d = 2V_T kT$$

$$\frac{\overline{V_o^2}}{\Delta f} = a + I_c b + I_c^{-2} c + I_c^{-1} d$$

$$\frac{\partial}{\partial I_c} \frac{\overline{V_o^2}}{\Delta f} = b - 2I_c^{-3} c - I_c^{-2} d$$

Minimum noise will be at a root of this equation

$$0 = \frac{Z_B R_s^2}{\beta} - \frac{8V_T^2 kTR}{I_c^3} - \frac{2V_T kT}{I_c^2}$$

$$\frac{Z_B R_s^2}{\beta} = \frac{8V_T^2 kTR}{I_c^3} - \frac{2V_T kT}{I_c^2}$$

4) a) cont'd

$$\frac{I_c^3 \beta R_s^2}{\beta} = 4V_t^2 kT - I_c V_t kT$$

$$\frac{I_c^3 \beta R_s^2}{\beta} + I_c V_t kT = 4V_t^2 kT$$

$$\frac{I_c^3 R_s^2}{\beta} + I_c V_t^2 = 4V_t^3 R$$

$$I_c^3 R_s^2 + I_c V_t^2 \beta = 4V_t^3 R \beta$$

Neglecting  $R$


$$I_c^3 R_s^2 + I_c V_t^2 \beta = 0$$

$$R_s = 1K \quad \beta = 200 \Rightarrow I_c = 0 ?$$

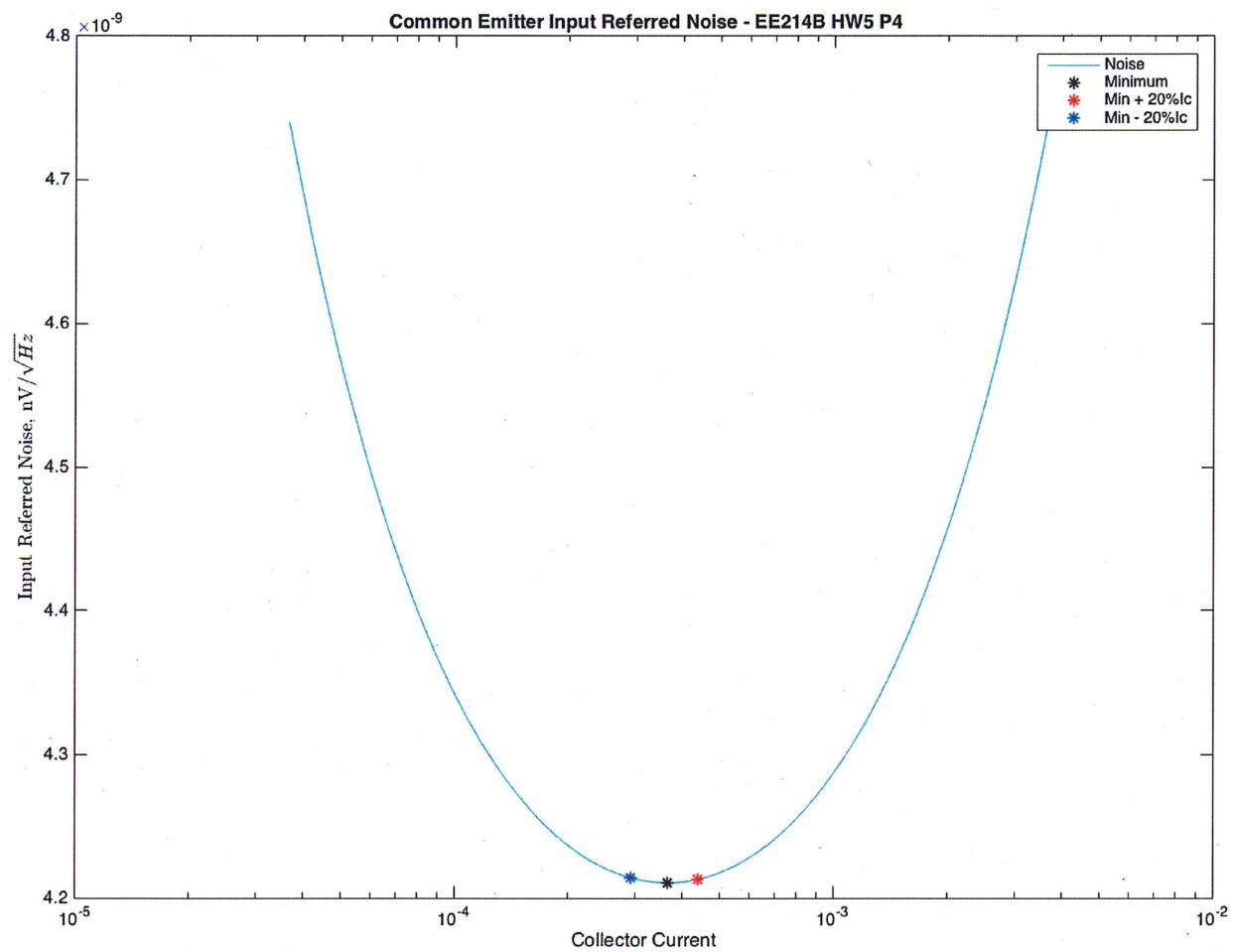b) Plot attached

$$\text{Error } I_c + 20_0 \text{P} - 0.055 \text{A}$$

$$\text{Error } I_c - 20_0 \text{P} - 0.082 \text{A}$$




5) CE &amp; CS Stages

Noise due to transistor and  $R_s$ 

a) Input source referred voltage noise

$$\frac{\overline{V_s^2}}{\Delta f} = 4kT \left( R_s + R_{b\beta} + \frac{g_m}{2\beta} \frac{(R_s + R_{b\beta})^2}{zg_m} + \frac{1}{zg_m^2} \right)$$

b)

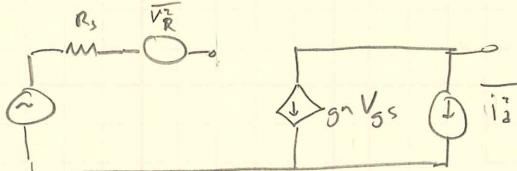

$$\frac{\overline{V_R^2}}{\Delta f} = 4kT R_s$$

$$\frac{\overline{i_d^2}}{\Delta f} = 4kT \delta g_m$$

$$\frac{\overline{V_s^2}}{\Delta f} = \frac{\overline{V_R^2}}{\Delta f} + \frac{\overline{V_d^2}}{\Delta f}$$

$$\frac{\overline{V_d^2}}{\Delta f} = \frac{\overline{i_d^2}}{\Delta f} \cdot \frac{1}{g_m^2}$$

$$\frac{\overline{V_s^2}}{\Delta f} = 4kT R_s + \frac{4kT \delta}{g_m} = 4kT \left( R_s + \frac{\delta}{g_m} \right)$$

c)  $R_s = 10 - 100\Omega$     $I_c = 1mA$     $r_b = 0$ .    $\beta = 300$     $T = 300$   
 $I_d = 1mA$     $g_m/I_d = 15$     $\gamma = .85$

Find value of  $R_s$  for  $\text{BJT} > \text{MOSFET}$  noise.BJT inferior to MOSFET at  $R_s = 813\Omega$ d) New value:  $R_s = 511\Omega$ 

e)  $R_s + r_b + \frac{g_m (R_s + r_b)^2}{2\beta} + \frac{1}{zg_m} = R_s + \frac{\delta}{g_m}$   
 $R_s \rightarrow 0$

$$r_b + \frac{g_m}{2\beta} \cdot r_b^2 + \frac{1}{zg_m} = \delta \quad \frac{\delta}{g_m \text{ mos}}$$

$$r_b^2 \frac{g_m}{2\beta} + r_b + \left( \frac{1}{zg_m} - \frac{\delta}{g_m} \right) = 0$$


$$a = \frac{g_m}{2\beta} \quad b = 1 \quad c = \frac{1}{zg_m} - \frac{\delta}{g_m}$$

$$r_b = 43.6\Omega$$

$$6) I_{C_1} = I_{C_2} = 1mA \quad \beta = \alpha \Rightarrow r_{\pi} = \infty$$

$$r_{b_1} = r_{b_2} = \infty$$

$$R_S = 5k\Omega = R$$

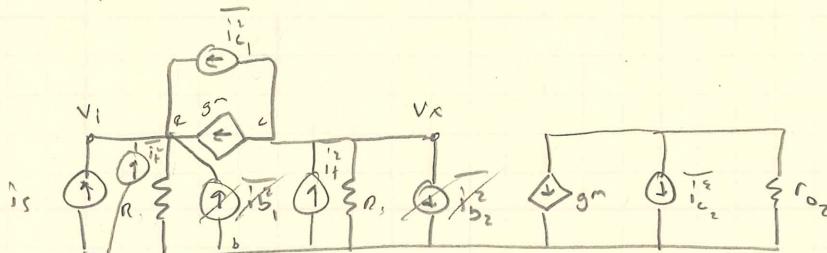

$$g_m = \frac{I_c}{V_t} = 38mS \text{ as } \beta \rightarrow \infty \quad i_b \rightarrow 0 \quad \text{hence } \overline{i_b^2} \rightarrow 0$$

$$\frac{1}{g_m} \Rightarrow 26\Omega$$

$$\overline{i_{R_1}^2} = \frac{4kT}{R} \quad \overline{i_c^2} = 2g_m I_c \quad \overline{i_b^2} = 0 \quad \text{output } g_m i_o = g_m r_{o_2} = \frac{g_m V_A}{I_c}$$

$$M_1 \text{ input impedance} = \frac{1}{g_m} \quad M_1 \text{ output impedance} = r_o = \infty$$

$$\frac{\overline{V_x}}{R} = i_s + g_m V_i$$

$$V_x \text{ referred to } i_{c_1} \text{ noise} = \frac{\overline{i_{c_1}^2}}{g_m^2}$$

$$\text{First stage gain } A_{v_o} \quad A_{v_o} = 1$$

$$V_x = R \cdot I_{C_1} \quad I_{C_1} \rightarrow \text{current divider} \quad I_c = \frac{1}{g_m} + R' I_o$$

$$\frac{V_x}{R} = \frac{R^2}{\frac{1}{g_m} + R} \quad I_s \approx R \overline{i_s}$$

$i_s$  referred  $V_x$  noise

$$\overline{i_{x_i}^2} = \frac{\overline{V_x^2}}{R^2}$$

$$\overline{i_{r_{T_1}}^2} = 3.312 \mu A^2 / Hz \quad \overline{i_{r_{T_2}}^2} = \frac{\overline{i_{r_{T_1}}^2}}{R^2} \approx 0$$

$$\overline{i_{c_1}^2} = 320 \mu A^2 / Hz$$

$$\overline{i_{c_2}^2} = \frac{\overline{i_{c_1}^2}}{g_m^2 R^2} = 0.87 \mu A^2 / Hz \approx 0$$

$$\text{Total input referred noise} = \sqrt{\overline{i_{x_i}^2} + \overline{i_{r_{T_1}}^2}} = 13 \mu A / \sqrt{Hz}$$

$$b) \text{ SNR} = 20 \text{dB} \quad \text{BW} = 150 \text{MHz}$$

$$\text{noise power} = 220 \text{nA rms}$$

$$20 \text{dB} = 20 \log\left(\frac{\text{rms Signal}}{220 \text{nA rms}}\right) \Rightarrow 10 = \frac{\text{Sis}}{220 \text{nA rms}}$$

$$\text{Signal power} = 2200 \text{nA rms}$$