



HOMEWORK ROUTE FORM

Stanford Center for Professional Development Student Information

Course No. Faculty / Instructor Name Date

Student Name Phone

Company Email

City State Country

Check One: ☒ Homework #: ☐ Midterm ☐ Other

The email address provided on this form will be used to return homework, exams, and other documents and correspondence that require routing.

Total number of pages faxed including cover sheet

For Stanford Use Only		
<hr/> <p>Date Received by the Stanford Center for Professional Development</p>	<hr/> <p>Date Instructor returned graded project</p>	<hr/> <p>Date the Stanford Center for Professional Development returned graded project:</p>
<hr/> <p>Score/Grade: (to be completed by instructor or by teaching assistant)</p>		

Please attach this route form to ALL MATERIALS and submit ALL to:

Stanford Center for Professional Development

496 Lomita Mall, Durand Building, Rm 410, Stanford, CA 94305-4036

Office 650.725.3015 | Fax 650.736.1266 or 650.725.4138

For homework confirmation, email scpd-distribution@lists.stanford.edu

<http://scpd.stanford.edu>

1. $\left\{ \frac{f_T}{I_D/W} \right\}$ for $\left\{ \begin{matrix} 0.18\mu m \\ 0.36\mu m \end{matrix} \right\}$ NMOS & PMOS at $8\frac{S}{A}$

		NMOS	PMOS	$\frac{NMOS}{PMOS}$
$0.18\mu m$	f_T	$26.4 GHz$	$8.87 GHz$	2.97
	I_D/W	$42.5 \frac{\mu A}{m}$	$15.1 \frac{\mu A}{m}$	2.81
$0.36\mu m$	f_T	$7.89 GHz$	$2.19 GHz$	3.58
	I_D/W	$20.57 \frac{\mu A}{m}$	$5.90 \frac{\mu A}{m}$	3.48
$\frac{0.36\mu m}{0.18\mu m}$	f_T	0.299	0.246	
	I_D/W	0.484	0.391	

$f_T \approx \frac{3}{2} \frac{\mu_{n,p} V_{ov}}{L_2}$ hence expect $f_T \propto \frac{1}{L^2} \rightarrow$ ratio expected to be $\boxed{\frac{1}{4}}$

$I_D/W \propto \frac{g_m}{I_D}$ hence for $2\times$ length expect current density to be $\boxed{\frac{1}{2}}$

2. $g_m/I_D = 7 \frac{S}{A}$ all passives the same

Specs:

$$R_L = 1k \quad C_L = 50 fF \quad R_S = 10k \quad A_{V_0} = -4 \quad L = 0.18 \mu m$$

a.) Find required tail current

$$\frac{g_m}{I_D} = 7 \frac{S}{A} \quad A_{V_0} = -4 = -g_m \cdot R_L \quad g_m = \frac{-A_{V_0}}{R_L} = 4 mS$$

$$I_D = \frac{g_m}{g_m/I_D} = 571 \mu A = I_{Tail}/2$$

$$I_{Tail} = 1142 \mu A$$

b) $I_D/\mu = 52 A/\mu m \quad I_D = 571 \mu A \quad W = I_D/I_D/\mu = 10.97 \mu m$

c) $f_T = 28 GHz$

$$C_{gg} = \frac{1}{2\pi} \cdot \frac{g_m}{f_T} = \frac{g_m}{\omega_T} = 22.5 fF$$

$$C_{gs} = \frac{C_{gd}}{C_{gg}} \cdot C_{gg} = 5.27 fF \quad C_{dd} = \frac{C_{dd}}{C_{gg}} \cdot C_{gg} = 13.3 fF$$

$$C_{gs} = C_{gs} - C_{gd} = 17.2 fF \quad C_{db} = C_{dd} - C_{gd} = 8.0 fF$$

Open Circuit Time Constant

$$\tau_1 = C_{gs} \cdot R_S \quad \tau_2 = C_{gd} (1 + |A_{V_0}|) \cdot R_S \quad \tau_3 = R_L \cdot (C_L + C_{db})$$

$$\text{Pole OCT} = 322 MHz$$


d) $C_{gs} = 18.3 fF \quad C_{gd} = 7.20 fF \quad C_{gg} = C_{gs} + C_{gd} = 25.5 fF$

e) Printout of .op attached
Printout of log-log plot attached

Simulation bandwidth 359 MHz, -10.3 dB error in calculation

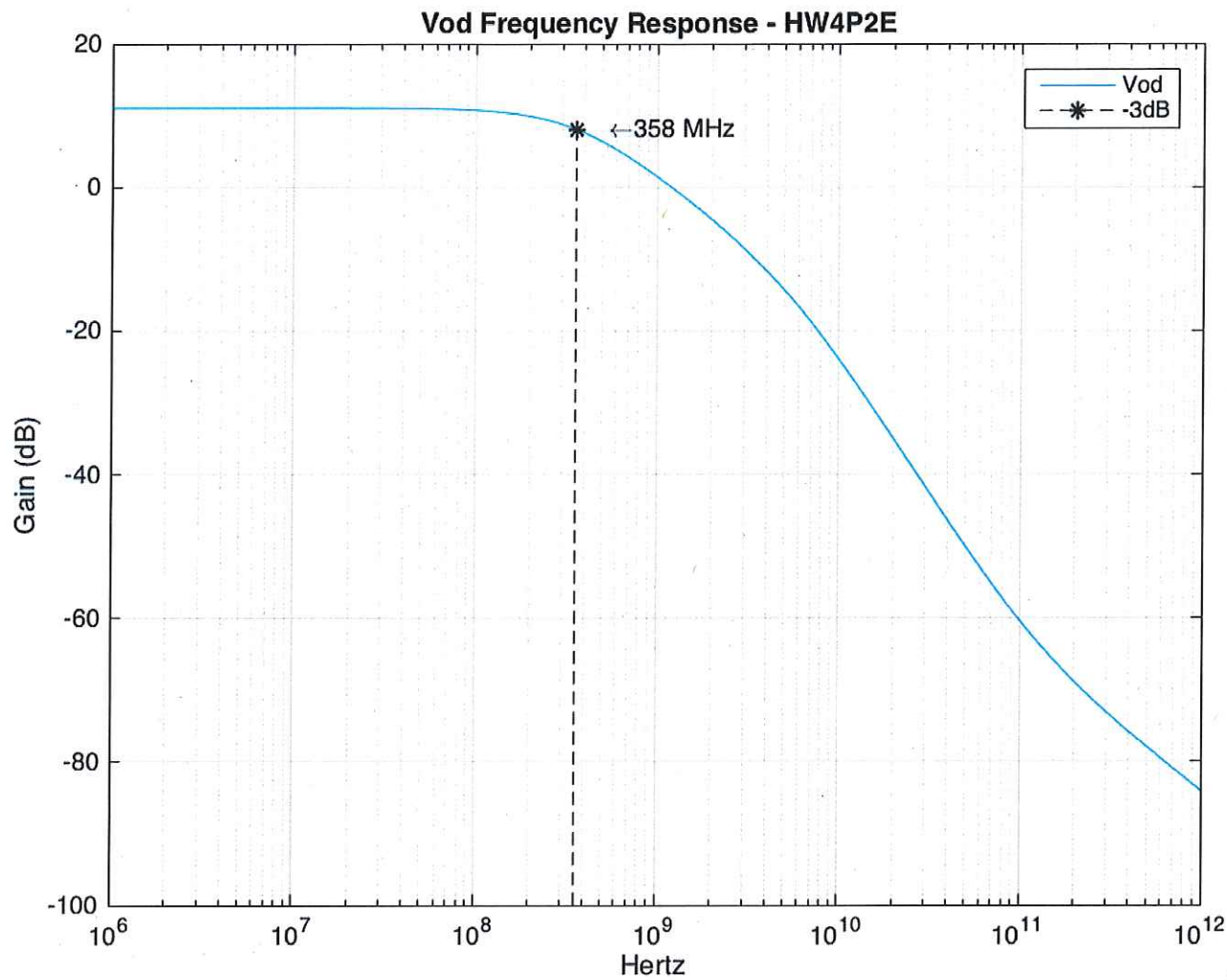f) $\frac{f_{TDB}}{I_{Tail}} = 31.4 GHz/A \quad 7 \frac{S}{A}$

$$\frac{f_{TDB}}{I_{Tail}} = 358 GHz/A \quad 13.3 \frac{S}{A} \leftarrow \text{more efficient class ex}$$



Problem 2 Part E

**** mosfets

subckt		
element	0:m1	0:m2
model	0:nmos214	0:nmos214
region	Saturati	Saturati
id	571.0000u	571.0000u
ibs	0.	0.
ibd	0.	0.
vgs	783.0706m	783.0706m
vds	1.0121	1.0121
vbs	-216.9294m	-216.9294m
vth	541.1596m	541.1596m
vdsat	176.8482m	176.8482m
vod	241.9110m	241.9110m
beta	22.0948m	22.0948m
gam eff	583.6854m	583.6854m
gm	4.0170m	4.0170m
gds	123.2972u	123.2972u
gmb	887.5677u	887.5677u
cdtot	12.6847f	12.6847f
cgtot	22.4760f	22.4760f
cstot	25.7820f	25.7820f
cbtot	19.4629f	19.4629f
cgs	16.2104f	16.2104f
cgd	5.2983f	5.2983f


3. DC Gain $A_v = 1$ $f_{3dB} = 1.1 \text{ GHz}$ $C_L = 500 \text{ fF}$ minimum $I_{T,1}$ $R_S = 0$
 $L_p = L_n = 0.24 \mu\text{m}$ $V_{IC} = 1.2 \text{ V}$ $V_{DD} = 1.8 \text{ V}$

a) Low freq half ckt



$$R_L = \frac{1}{g_{mP}} \quad A_{v0} = - \frac{g_{mN}}{g_{mP} \parallel r_o} \approx - \frac{g_{mN}}{g_{mP}}$$

b) Small sckt

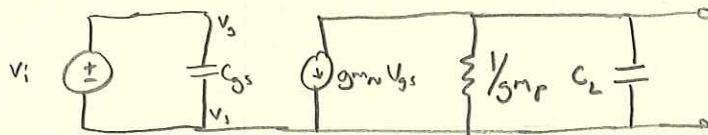

$$f_{3dB} = \frac{1}{2\pi C_L / g_{mP}} = \frac{g_{mP}}{2\pi C_L} \quad g_{mP} = f_{3dB} \cdot 2\pi C_L = 3.5 \text{ mS}$$

c) $\frac{g_{mP}}{I_D} = 8 \frac{\text{S}}{\text{A}} \quad I_{D,P} = I_{D,N} \quad g_{mP} = g_{mN} \Rightarrow \frac{g_{mN}}{I_D} = \frac{g_{mP}}{I_D} = 8$

Find I_{SS} and device widths

$$I_D = \frac{g_{mP}}{\frac{g_{mP}}{I_D}} = 432 \mu\text{A} \Rightarrow I_{SS} = 864 \mu\text{A}$$

$$W_N = \frac{I_D}{I_D / W_N} = 13.76 \mu\text{m} \quad W_P = 43 \mu\text{m}$$

d) -3dB BW: 903 MHz

AC Response and op list attached

e) $K = \frac{1}{2 - \frac{1.1 \text{ GHz}}{903 \text{ MHz}}} = 1.2682$

f) $I_{SS} = 1.095 \text{ mA} \quad f_{3dB} = 1.091 \text{ GHz}$

$$g_m = 4.392 \quad I_D = 547 \mu\text{A} \quad \frac{g_m}{I_D} = 8.021 \rightarrow \text{unchanged}$$

3. g) $\frac{g_m}{I_D} \propto \frac{I_D}{\omega}$ hence $\frac{g_m}{I_D} < \frac{\kappa I_D}{\kappa \omega}$

for constant $\frac{g_m}{I_D}$, increasing I_D results in increasing g_m
 constant $\frac{g_m}{I_D}$ leads to constant f_T but increasing I_D
 means that the fraction of C_{load} determining the total
 capacitance is decreasing, hence f_{p1} increases

h) With $A_v = 1$ the C_{gsN} capacitor is bootstrapped. With a $R_S = 0$
 C_{gsN} is not considered. Hence C_{dbN} is the only drain connected
 NMOS cap left. C_{gsP} is shunted, hence we need to consider
 C_{dbP} and C_{gsP} .


Plot attached.

I_{SS} converged to 1154 μA final ratio 1.33

i) PMOS width = 54.4 μm NMOS width = 18.4 μm

j) Bandwidth:

Plot and .op list attached.

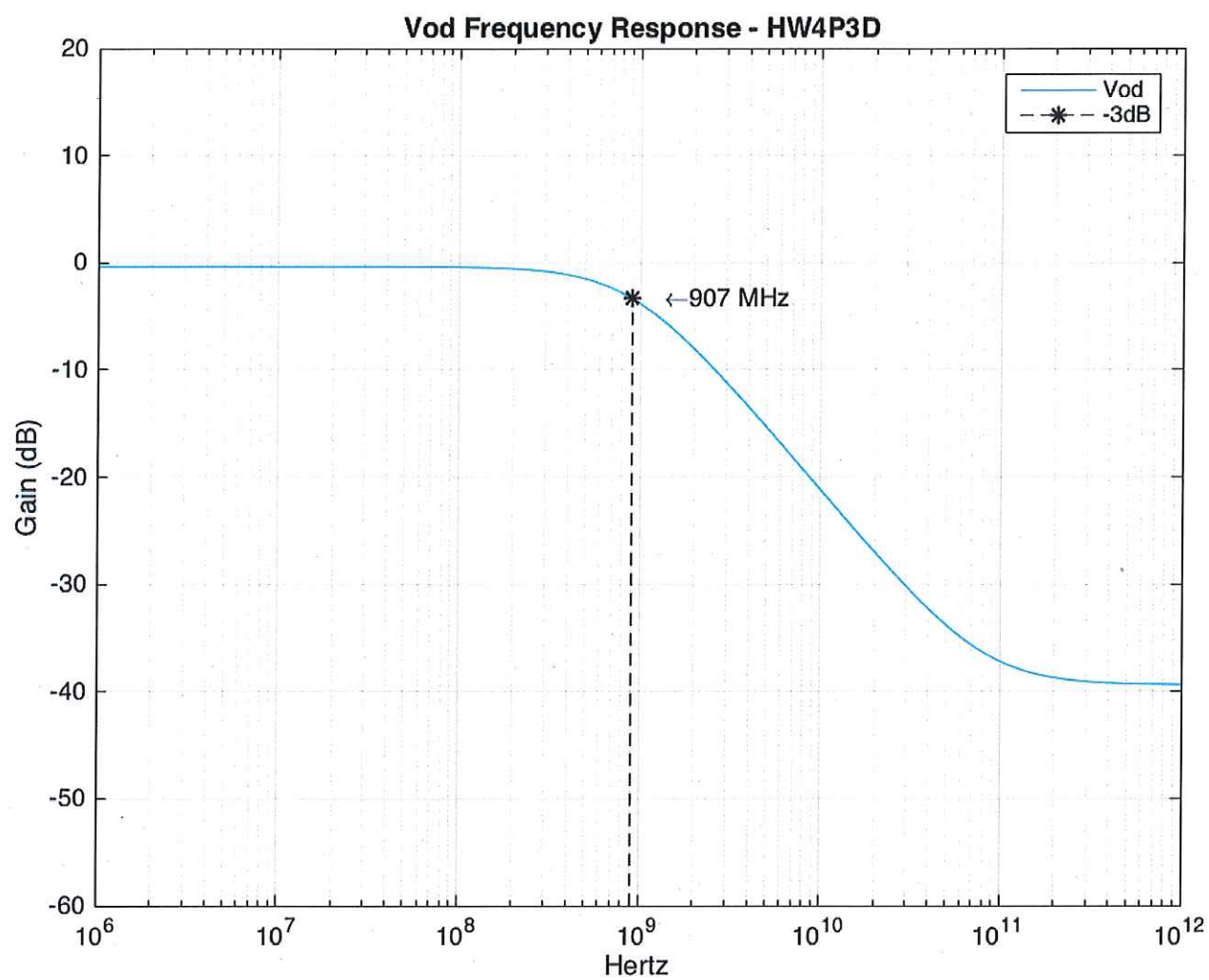

Problem 3 Part D

**** mosfets


subckt


element	0:mn1	0:mn2	0:mp1	0:mp2
model	0:nmos214	0:nmos214	0:pmos214	0:pmos214
region	Saturati	Saturati	Saturati	Saturati
id	547.7760u	547.7760u	-547.7760u	-547.7760u
ibs	0.	0.	0.	0.
ibd	0.	0.	0.	0.
vgs	766.8026m	766.8026m	-705.2563m	-705.2563m
vds	861.5463m	861.5463m	-705.2563m	-705.2563m
vbs	-233.1974m	-233.1974m	0.	0.
vth	539.3613m	539.3613m	-473.2138m	-473.2138m
vdsat	176.0868m	176.0868m	-201.6380m	-201.6380m
vod	227.4413m	227.4413m	-232.0425m	-232.0425m
beta	24.8611m	24.8611m	20.9143m	20.9143m
gam eff	584.3111m	584.3111m	535.9921m	535.9921m
gm	4.3913m	4.3913m	4.3583m	4.3583m
gds	89.8445u	89.8445u	126.0953u	126.0953u
gmb	1.0058m	1.0058m	1.3630m	1.3630m
cdtot	20.2688f	20.2688f	76.9346f	76.9346f
cgtot	43.0812f	43.0812f	141.0176f	141.0176f
cstot	48.3107f	48.3107f	159.6900f	159.6900f
cbtot	32.8565f	32.8565f	113.7785f	113.7785f
cgs	32.7243f	32.7243f	102.1611f	102.1611f
cgd	8.3798f	8.3798f	35.5343f	35.5343f

Problem 3 Part F

**** mosfets

subckt				
element	0:mn1	0:mn2	0:mp1	0:mp2
model	0:nmos214	0:nmos214	0:pmos214	0:pmos214
region	Saturati	Saturati	Saturati	Saturati
id	547.7760u	547.7760u	-547.7760u	-547.7760u
ibs	0.	0.	0.	0.
ibd	0.	0.	0.	0.
vgs	766.8026m	766.8026m	-705.2563m	-705.2563m
vds	861.5463m	861.5463m	-705.2563m	-705.2563m
vbs	-233.1974m	-233.1974m	0.	0.
vth	539.3613m	539.3613m	-473.2138m	-473.2138m
vdsat	176.0868m	176.0868m	-201.6380m	-201.6380m
vod	227.4413m	227.4413m	-232.0425m	-232.0425m
beta	24.8611m	24.8611m	20.9143m	20.9143m
gam eff	584.3111m	584.3111m	535.9921m	535.9921m
gm	4.3913m	4.3913m	4.3583m	4.3583m
gds	89.8445u	89.8445u	126.0953u	126.0953u
gmb	1.0058m	1.0058m	1.3630m	1.3630m
cdtot	20.2688f	20.2688f	76.9346f	76.9346f
cgtot	43.0812f	43.0812f	141.0176f	141.0176f
cstot	48.3107f	48.3107f	159.6900f	159.6900f
cbtot	32.8565f	32.8565f	113.7785f	113.7785f
cgs	32.7243f	32.7243f	102.1611f	102.1611f
cgd	8.3798f	8.3798f	35.5343f	35.5343f

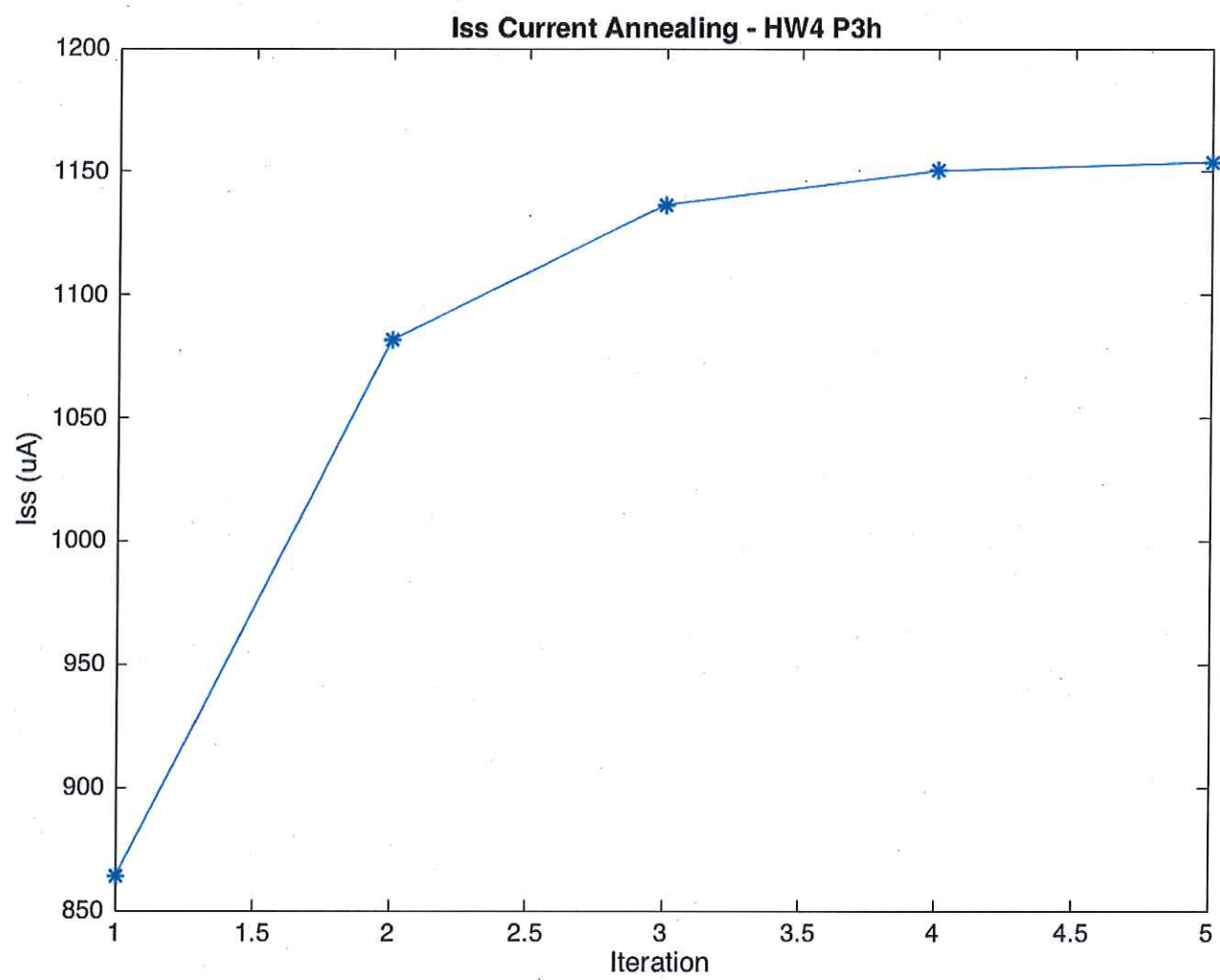

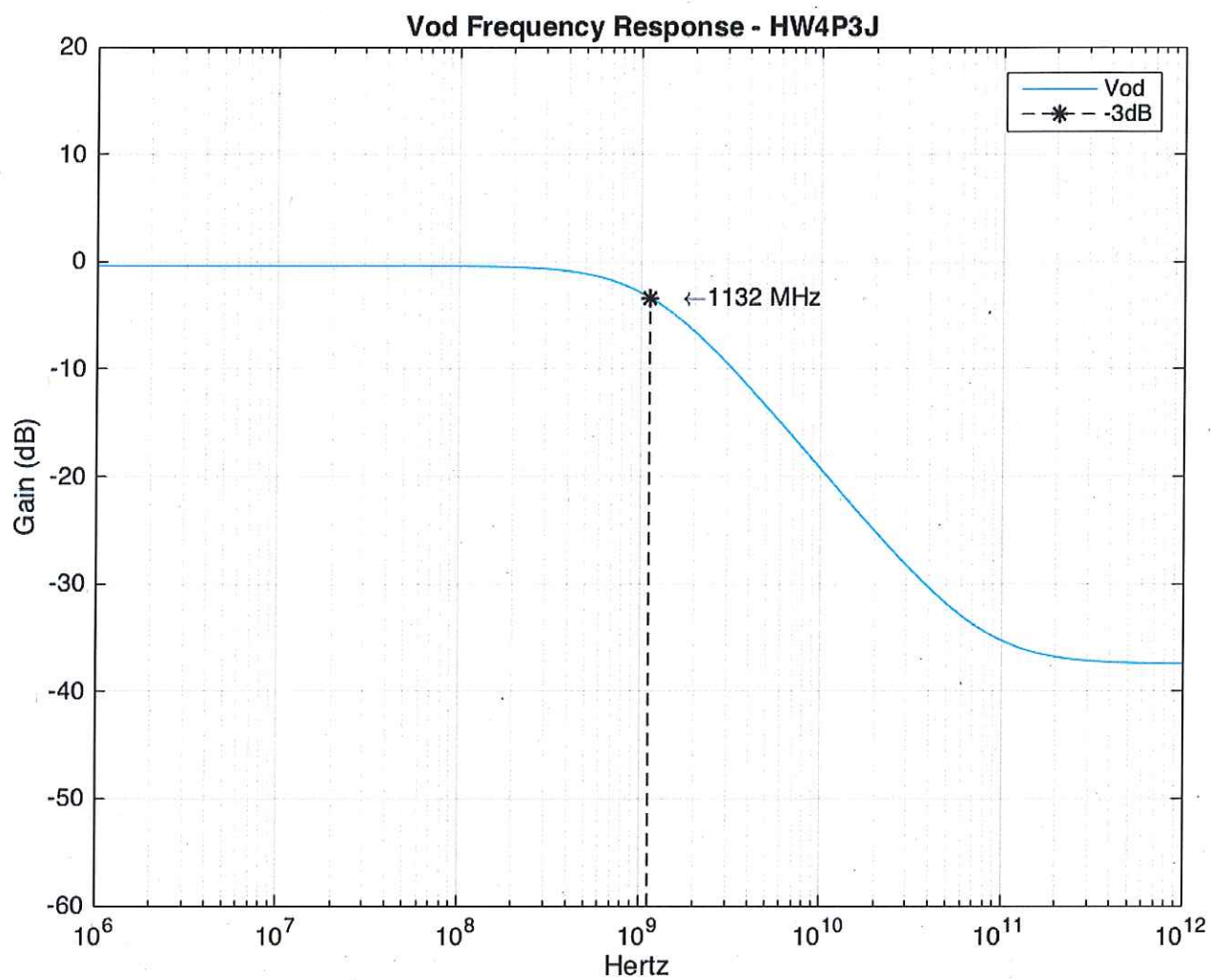

Problem 3 Part J


**** mosfets


```

subckt
element 0:mn1      0:mn2      0:mp1      0:mp2
model    0:nmos214  0:nmos214  0:pmos214  0:pmos214
region   Saturati   Saturati   Saturati   Saturati
id       577.0000u  577.0000u  -577.0000u  -577.0000u
ibs      0.         0.         0.         0.
ibd      0.         0.         0.         0.
vgs      766.9958m  766.9958m  -705.3199m  -705.3199m
vds      861.6758m  861.6758m  -705.3199m  -705.3199m
vbs     -233.0042m  -233.0042m   0.         0.
vth      539.3270m  539.3270m  -473.2214m  -473.2214m
vdsat    176.2447m  176.2447m  -201.7064m  -201.7064m
vod      227.6688m  227.6688m  -232.0985m  -232.0985m
beta     26.1364m   26.1364m   22.0171m   22.0171m
gam eff  584.3389m  584.3389m  536.0068m  536.0068m
gm        4.6204m   4.6204m   4.5895m   4.5895m
gds      94.5421u   94.5421u  132.8016u  132.8016u
gmb       1.0584m   1.0584m   1.4355m   1.4355m
cdtot    21.3001f   21.3001f   80.9822f   80.9822f
cgtot    45.3017f   45.3017f  148.4556f  148.4556f
cstot    50.7881f   50.7881f  168.1033f  168.1033f
cbtot    34.5234f   34.5234f  119.7571f  119.7571f
cgs      34.4107f   34.4107f  107.5503f  107.5503f
cgd       8.8119f   8.8119f   37.4090f   37.4090f

```

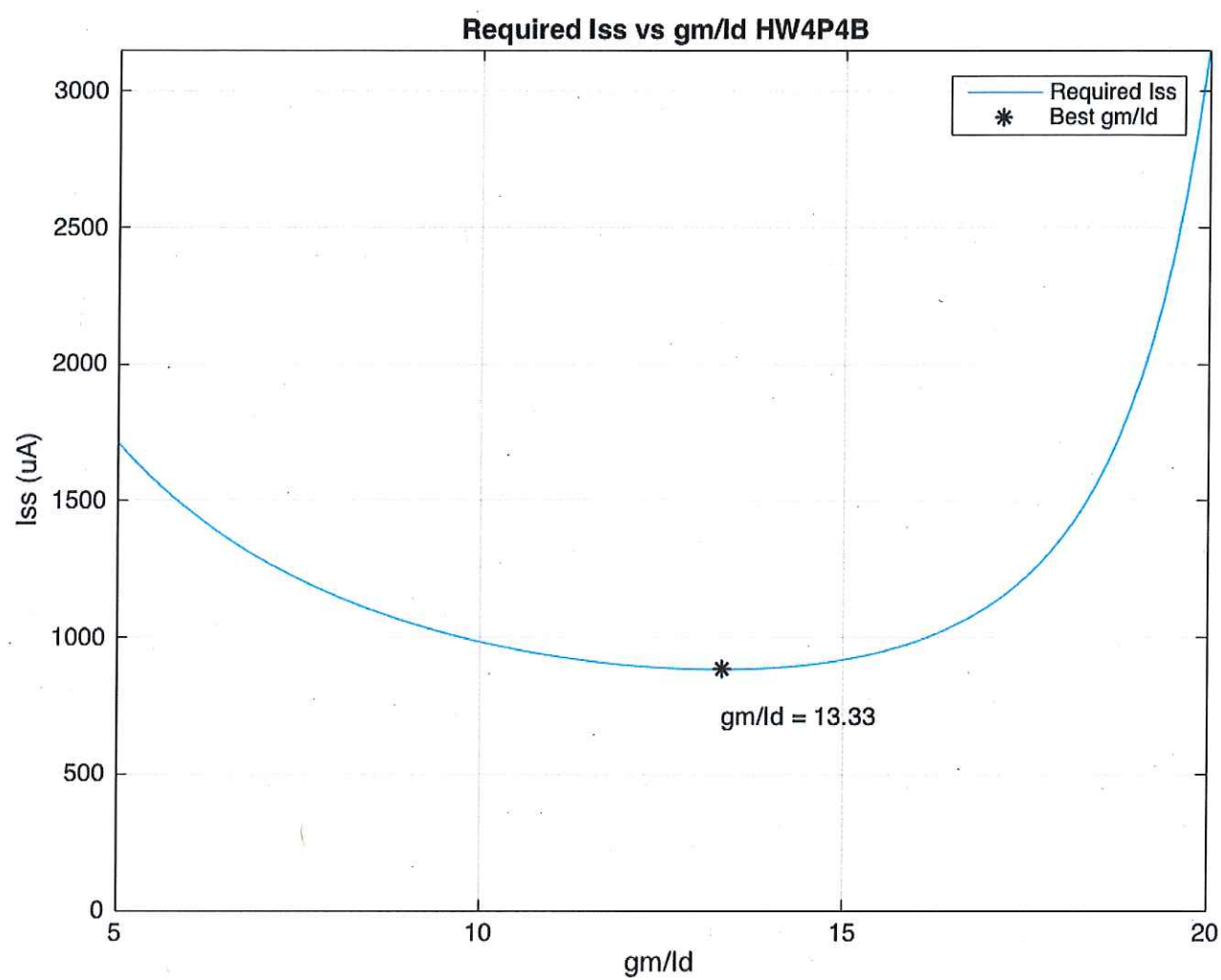4. b) Plot attached
- c) $N_{\text{mos}} : 33.2 \mu\text{m}$
 $P_{\text{mos}} : 124.0 \mu\text{m}$
- d.) Printout & plot attached



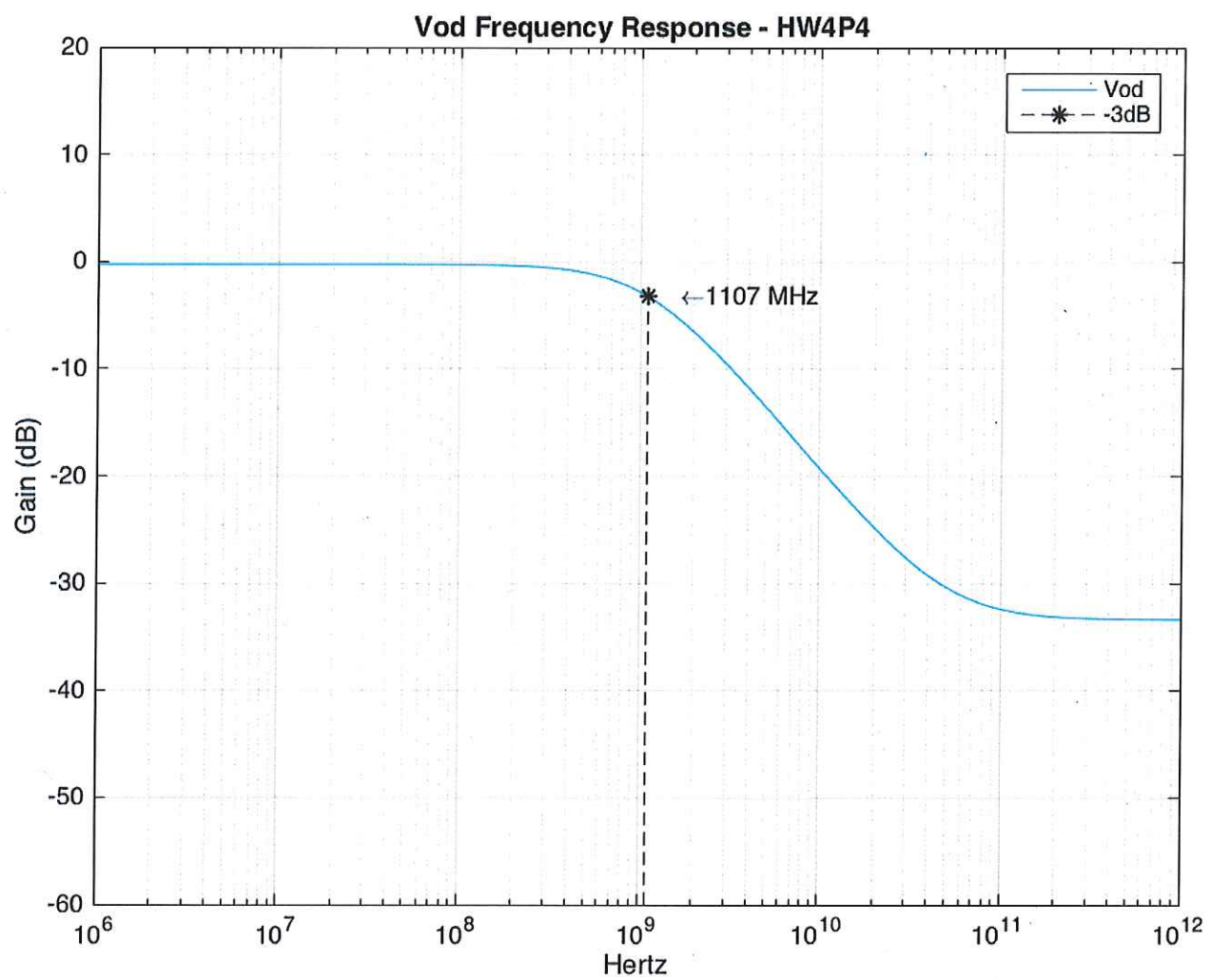

Problem 4 Part D

**** mosfets



```

subckt
element 0:mn1      0:mn2      0:mp1      0:mp2
model    0:nmos214  0:nmos214  0:pmos214  0:pmos214
region   Saturati   Saturati   Saturati   Saturati
id       442.0000u  442.0000u -442.0000u -442.0000u
ibs      0.         0.         0.         0.
ibd      0.         0.         0.         0.
vgs      689.1093m  689.1093m -607.5475m -607.5475m
vds      881.5618m  881.5618m -607.5475m -607.5475m
vbs     -310.8907m -310.8907m  0.         0.
vth      558.9171m  558.9171m -473.7236m -473.7236m
vdsat    117.8577m  117.8577m -127.0213m -127.0213m
vod      130.1922m  130.1922m -133.8239m -133.8239m
beta     54.1946m   54.1946m   48.5372m   48.5372m
gam eff  584.3667m  584.3667m  536.1561m  536.1561m
gm       5.9555m    5.9555m    5.8582m    5.8582m
gds     107.8540u   107.8540u  141.0537u  141.0537u
gmb      1.3490m    1.3490m    1.8036m    1.8036m
cdtot    43.5573f   43.5573f   177.0913f   177.0913f
cgtot    93.0095f   93.0095f   317.8289f   317.8289f
cstot   102.9546f   102.9546f   358.7041f   358.7041f
cbtot    69.7235f   69.7235f   260.9957f   260.9957f
cgs      70.1527f   70.1527f   228.1761f   228.1761f
cgd     18.3062f    18.3062f    80.8248f    80.8248f

```

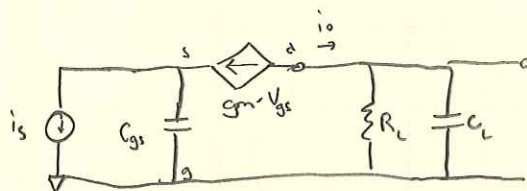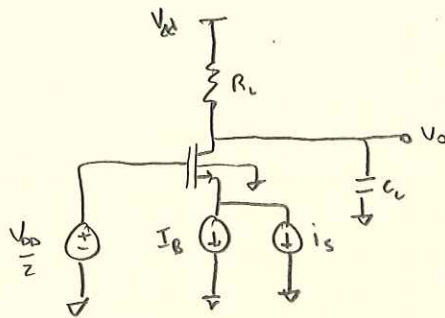5) a) $R_L = 6k$ $C_L = 100f$ $I_{B,iss} = 100\mu A$ $V_{DD} = 1.8V$ $L = 0.13\mu m$

Common gate stage - consider only C_{gs} & g_m



$$\text{input impedance} = \frac{1}{g_m} \parallel \frac{1}{sC_{gs}}$$

$$\text{output impedance} \approx r_o(1 + g_m R_L) \rightarrow \infty$$

$$\frac{i_o}{i_s} \approx \frac{1}{1 + s \frac{C_{gs}}{g_m}}$$

$$V_o \approx i_o \cdot \left(R_L \parallel \frac{1}{sC_L} \right) = i_o \cdot \frac{\frac{R_L}{sC_L}}{\frac{R_L}{sC_L} + \frac{1}{sC_L}} = i_o \cdot \frac{R_L}{1 + sR_L C_L}$$

$$V_o = \frac{1}{1 + s \frac{C_{gs}}{g_m}} \cdot \frac{R_L}{1 + sR_L C_L} \cdot i_s$$

b) $\frac{V_o}{i_s} = \frac{R_L}{\left(1 + s \frac{C_{gs}}{g_m}\right)(1 + sR_L C_L)}$

denominator

$$1 + s \frac{C_{gs}}{g_m} + s R_L C_L + s^2 C_{gs} C_L R_L / g_m$$

$$b_1 = C_{gs}/g_m + R_L C_L$$

$$b_2 = C_{gs} C_L R_L / g_m$$

$$\omega_{p1} = \frac{1}{b_1} \quad \omega_{p2} = \frac{1}{b_2}$$

5.) c) g_m/c_{gs} such that $\frac{\omega_{p2}}{\omega_{p1}} = 100$

$$\omega_{p2} \approx \frac{b_1}{b_2} \quad \omega_{p1} \approx \frac{1}{b_1}$$

$$\frac{\omega_{p2}}{\omega_{p1}} \approx \frac{b_1^2}{b_2} \Rightarrow b_1^2 = \left(\frac{C_{gs}}{g_m} + R_L C_L \right)^2 = \frac{C_{gs}^2}{g_m^2} + R_L^2 C_L^2 + \frac{2 C_{gs} C_L R_L}{g_m}$$


$$b_2 = \frac{C_{gs} C_L R_L}{g_m}$$

$$\frac{b_1^2}{b_2} = \frac{\frac{C_{gs}^2}{g_m^2}}{\frac{C_{gs} C_L R_L}{g_m}} + \frac{\frac{R_L^2 C_L^2}{g_m}}{\frac{C_{gs} C_L R_L}{g_m}} + \frac{\frac{2 C_{gs} C_L R_L}{g_m}}{\frac{C_{gs} C_L R_L}{g_m}}$$

$$= \frac{C_{gs}/g_m}{C_L R_L} + \frac{C_L R_L}{\frac{C_{gs}}{g_m}} + 2 = 2 + \frac{C_{gs}^2/g_m^2 + C_L^2 R_L^2}{C_L R_L C_{gs}/g_m} = 100$$

$$\frac{g_m}{C_{gs}} = \frac{1}{C_L R_L (49 + 70 \sqrt{6})} = \frac{0.163 \text{ nS}}{\text{fF}} = 163 \times 10^9 \frac{\text{S}}{\text{F}} = 1636 \text{ rad/s} = 266 \text{ Hz}$$

d) SS model from Ch4 Slide 8

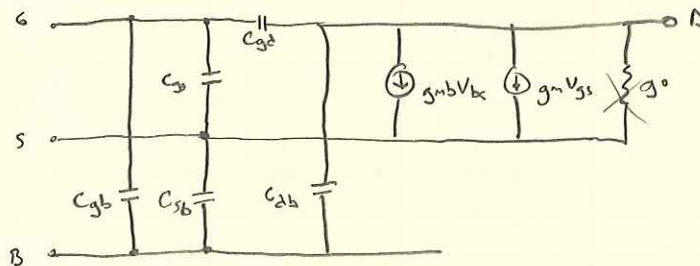


$$C_{gs} = C_{gs} + C_{gb} + C_{gd}$$

$$C_{db} = C_{db} + C_{gd}$$

$$V_g = 0 \quad V_b = 0 \Rightarrow V_{bs} = V_{gs} \quad g_m + g_{mb} = g_m'$$
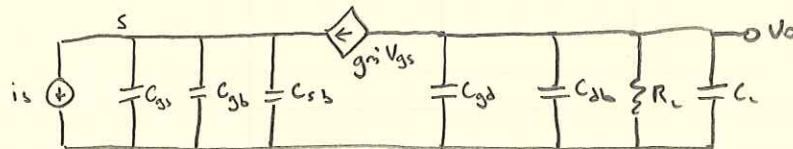
$$C_{gs} \parallel C_{gb} \parallel C_{sb} \quad C_{gd} \parallel C_{db} = C_{dd}$$



$$C_{in} = C_{gs} + C_{gb} + C_{sb}$$

$$C_{out} = C_{gd} + C_{db} + C_L$$

$$\frac{V_o}{i_s} = \frac{R_L}{\left(1 + s C_{in}\right) \left(1 + s C_{out} R_L\right)}$$

$$s) \quad e) \quad b_1 = \frac{C_{in}}{g_{m1}} + R_L C_{out} \quad b_2 = \frac{C_{in} C_{out} R_L}{g_{m1}}$$

$$\omega_{P2} \approx \frac{b_1}{b_2} = \frac{\frac{C_{in}}{g_{m1}}}{\frac{C_{in} C_{out} R_L}{g_{m1}}} + \frac{\frac{R_L C_{out}}{C_{in} C_{out} R_L}}{\frac{C_{in} C_{out} R_L}{g_{m1}}} = \frac{1}{C_{out} R_L} + \frac{g_{m1}}{C_{in}}$$

$$\omega_{P1} \approx \frac{1}{T_1} = \frac{1}{\frac{C_{in}}{g_{m1}} + R_L C_{out}}$$

$$C_{in} = C_{gs} + C_{gb} + C_{cb} \quad C_{out} = C_{gd} + C_{db} + C_L$$

$$C_{gs} = C_{gs} + C_{gs} + C_{gs}$$

$$C_{db} = C_{gd} + C_{db} \quad C_{ss} = C_{gs} + C_{sb}$$

$$C_{in} = C_{gs} + C_{sb} - C_{gd}$$

$$\frac{C_{db}}{C_{gs}} = \frac{C_{gd} + C_{db}}{C_{gs} + C_{gd} + C_{gb}}$$

$$C_{out} = C_{db} + C_L$$

$$\omega_T = \frac{g_m}{C_{gs}} \quad \frac{1}{\omega_T} = \frac{C_{gs}}{g_m}$$

$$R_L C_{out} = R_L C_{db} + R_L C_L$$

$$C_{db} = \frac{C_{db}}{C_{gs}} \cdot C_{gs} = \frac{C_{db}}{C_{gs}} \cdot \frac{g_m}{\omega_T} \cdot \frac{I_{bias}}{I_1}$$

$$\omega_{P1} \approx \frac{1}{R_L [C_L + \frac{C_{db}}{C_{gs}} \frac{1}{\omega_T} \frac{g_m}{I_1} I_{bias}]}$$

f) Plot attached

$$g) \quad \frac{I_d}{W} = 36.2 \mu A/\mu m \quad W = 2.76 \mu m \quad \omega_T = 156 \text{ Grad/s} \quad f_T = 24.8 \text{ GHz}$$

$$h) \quad g_m = 902 \mu S \quad I_d = 100 \mu A$$

$$\frac{g_m}{I_d} = 9.02$$

$$\omega_T = \frac{g_m}{C_{tot}} = 160 \text{ Grad/s}$$

$$C_{tot} = 5.626 \text{ fF}$$


These values are very close to the design point

$$i) \quad \omega_{P1 \text{ sim}} = 1.61 \text{ Grad/s}$$

$$\text{ratio} = 104.8 \quad \text{error} = -4.62^\circ$$

$$\omega_{P2 \text{ sim}} = 163.8 \text{ Grad/s}$$
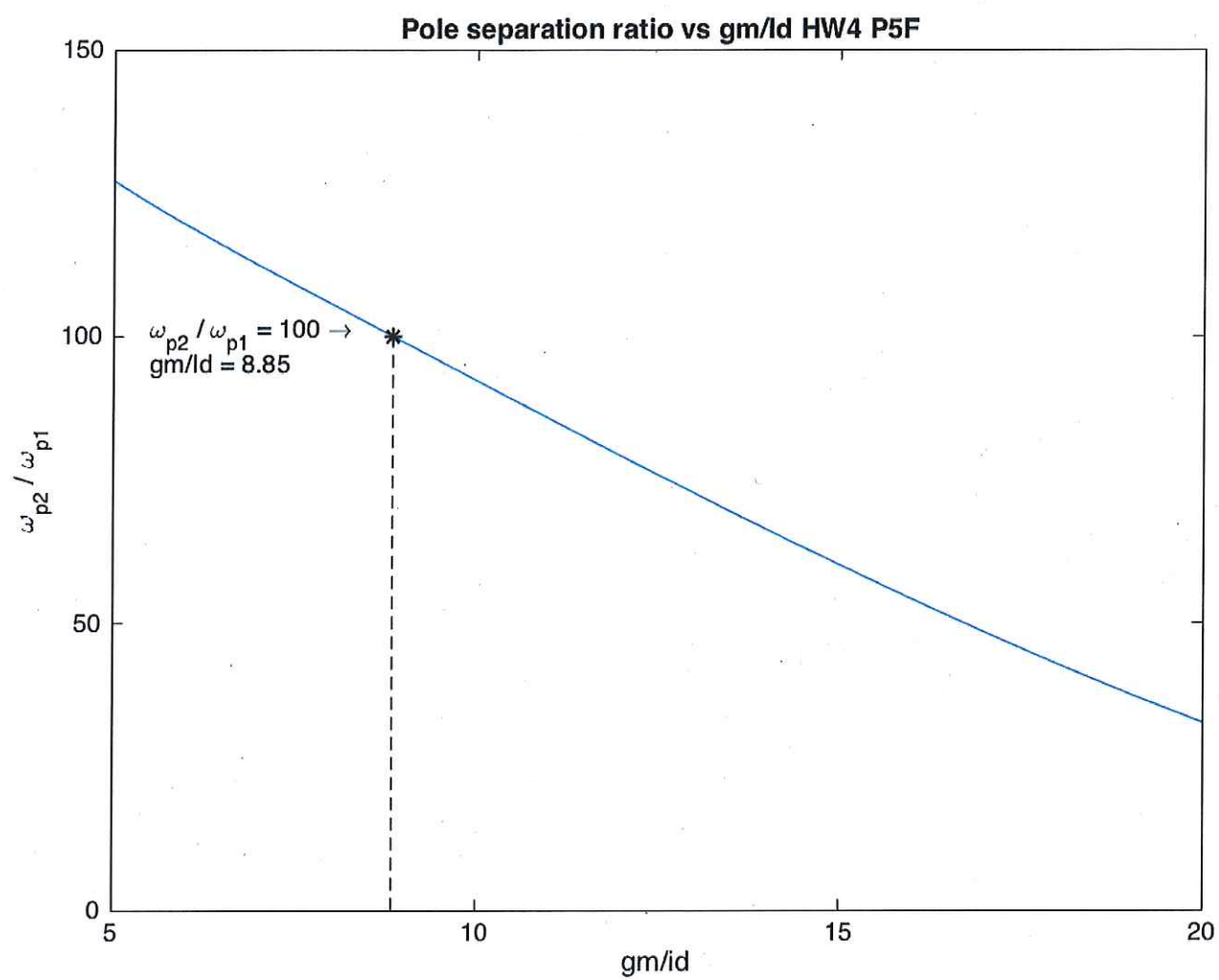
$$j) \quad \omega_T \text{ ptc} = 163 \text{ Grad/s} \quad \text{This was a very reasonable estimate.}$$



Problem 5 Part H

**** mosfets

```
subckt
element 0:mn1
model 0:nmos214
region Saturati
id 100.0000u
ibs 0.
ibd 0.
vgs 723.6087m
vds 1.0236
vbs -176.3913m
vth 528.9008m
vdsat 149.2505m
vod 194.7079m
beta 5.7016m
gam eff 580.2213m
gm 901.8837u
gds 25.8755u
gmb 201.3754u
cdtot 3.3806f
cgtot 5.6258f
cstot 6.6973f
cbtot 5.3412f
cgs 4.0470f
cgd 1.3242f
```